



ELIZADE UNIVERSITY, ILARA-MOKIN, ONDO STATE
FACULTY OF ENGINEERING
DEPARTMENT OF ELECTRICAL AND ELECTRONICS
ENGINEERING

FIRST SEMESTER EXAMINATION, 2020/2021 ACADEMIC SESSION

COURSE TITLE: Power Electronics and Drives

COURSE CODE: EEE 533

EXAMINATION DATE: March, 2021

COURSE LECTURER: Prof Dr. M.J.E. Salami

A rectangular box containing a handwritten signature in blue ink.

HOD's SIGNATURE

TIME ALLOWED: 2 HR and 30 minutes

INSTRUCTIONS:

1. ANSWER ANY FOUR (4) QUESTIONS
2. SEVERE PENALTIES APPLY FOR MISCONDUCT, CHEATING, POSSESSION OF UNAUTHORIZED MATERIALS DURING EXAM.
3. YOU ARE **NOT** ALLOWED TO BORROW CALCULATORS AND ANY OTHER WRITING MATERIALS DURING THE EXAMINATION.

Question 1 [15 Marks]

a) The current through a diode is shown in Fig. Q1a. Suppose $t_1 = 350 \mu s$, $t_2 = 500 \mu s$, $f = 200 \text{ Hz}$, $f_s = 5 \text{ kHz}$, $I_m = 450 \text{ A}$, and $I_a = 150 \text{ A}$, determine the:

(i) RMS current. (4 marks)

(ii) Average diode current. (2 marks)

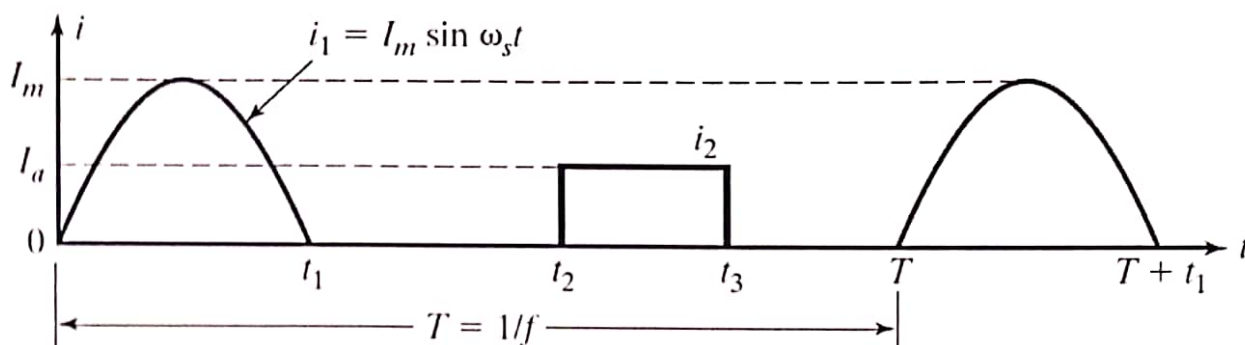


Fig. Q1a

b) Fig. Q1b shows a half-wave rectifier, having a freewheeling diode D_2 and RL load, where $R = 100 \Omega$ and $L = 25 \text{ mH}$, $V_m = 100 \text{ V}$, and the source frequency is 50 Hz .

(i) Sketch the waveforms $v_s(t)$, $i_o(t)$, i_{D1} and i_{D2} . (2 marks)

(ii) Obtain the Fourier series expression for the voltage across the load. (4 marks)

(iii) Determine the average load voltage and current. (3 marks)

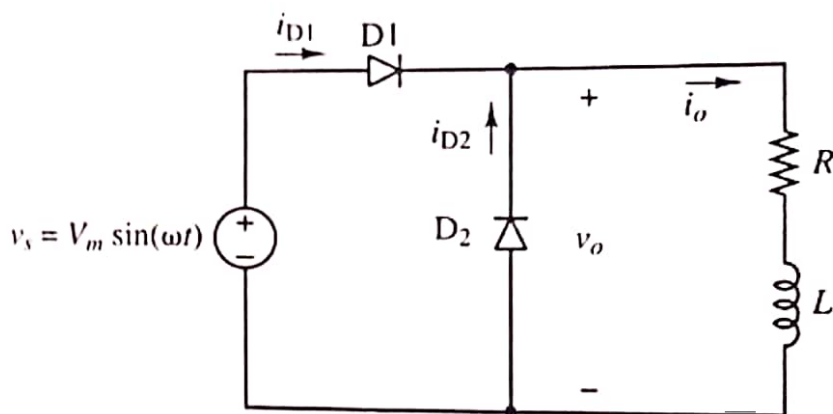


Fig. Q1b

Question 2 [15 Marks]

a) State the merits and demerits of using bridge circuit instead of center-tapped transformer for full wave single-phase rectifier. (3 marks)

b) Derive an expression for the:

i) Average output voltage (3 marks)

ii) Root mean square (RMS) output voltage (3 marks)

for a q-phase uncontrolled rectifier with resistive load and a supply voltage $V_s = V_m \sin \omega t$.

c) A six-phase uncontrolled star rectifier has a purely resistive load of $R = 10 \Omega$, the peak supply voltage, $V_m = 220 \text{ V}$ and the supply frequency $f = 50 \text{ Hz}$. Determine the

i) Average output voltage (3 marks)

ii) RMS output voltage (3 marks)

of the rectifier if the source inductance is negligible.

Question 3 [15 Mark]

a) i) Draw and explain the necessity of static and dynamic equalizing circuit for series connected thyristors. (3 marks)

ii) Derive expressions used for determining the values of shunt resistor R and capacitor C in this circuit. (4 marks)

- b) The voltage and current rating in a particular circuit are 3 kV and 750 A . Thyristors with rating of 800 V and 175 A are available. The recommended minimum derating factor is 15% . Calculate the
- Number of series and parallel units required. (4 marks)
 - Required values of R and C used in the static and dynamic equalizing circuits, if the maximum forward leakage current for the thyristors is 10 mA and $\Delta Q = 20\text{ }\mu\text{C}$. (4 marks)

Question 4 [15 Marks]

- a) State the advantages and disadvantages of phase-controlled rectifiers over the uncontrolled rectifiers. (2 marks)
- b) Derive expression for the
- Average output voltage (2 marks)
 - RMS output voltage (3 marks)
- for the single-phase, phase-controlled rectifier. Assume the supply voltage is $V_s = V_m \sin \omega t$ and that the firing (delay) angle is α .
- c) Fig.Q4c shows a single-phase half-wave converter which is operated from a $220\text{ V } 50\text{ Hz}$ supply and the resistive load is $R = 10\text{ }\Omega$. Suppose the average output load is 25% of the maximum possible average output voltage, calculate the
- Delay angle (2 marks)
 - RMS and average output currents (2 marks)
 - Average and RMS thyristors currents (2 marks)
 - Input power factor. (2 marks)

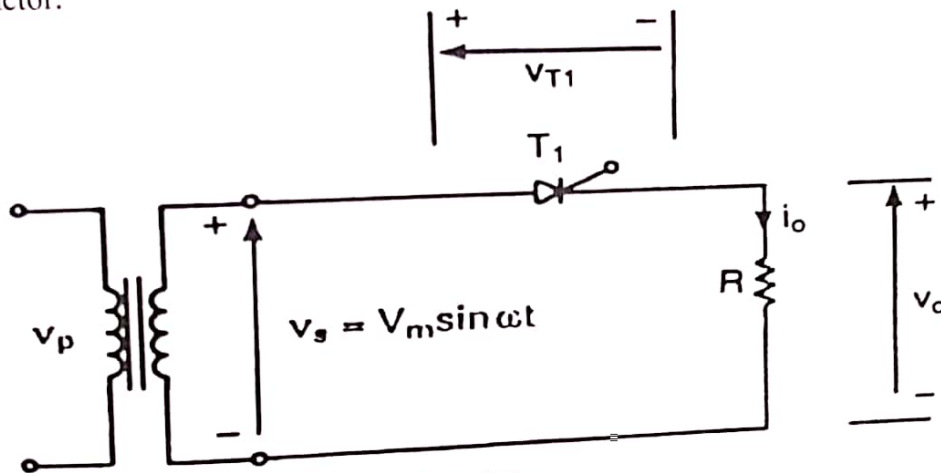


Fig. Q4c

Question 5 [15 Marks]

- a) Explain the following terms with respect to phase-control converter;
- Semiconverter (1 mark)
 - Full converter (1 mark)
 - Dual converter (1 mark)
- State the applications of each of these converters.
- b) Derive expression for the average output voltage and RMS output voltage for a three-phase phase-controlled half-wave converter in terms of delay angle α and peak supply voltage V_m . (4 marks)
- c) Fig.Q5c shows a three-phase half-wave phase-control converter which is operated from a three-phase Y -connected $440\text{ V } 50\text{ Hz}$ supply. Suppose it is required to obtain an average output voltage of 50% of the maximum possible output voltage, calculate the
- Delay angle, α . (2 marks)
 - Average and RMS output currents. (2 marks)
 - Average and RMS thyristors currents (2 marks)
 - Rectification efficiency (2 marks)

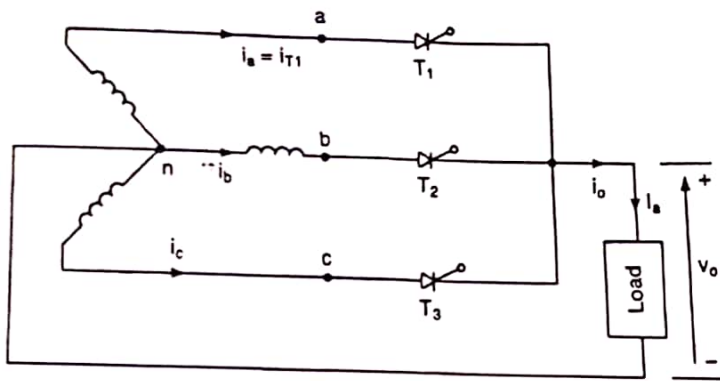


Fig. Q5c

Question 6 [15 Marks]

- a) Design the triggering circuit of Fig. Q6a in which the parameters of the Unijunction Transistor (UJT) are $V_s = 30 V$, $\eta = 0.51$, $I_p = 10 \mu A$, $V_v = 3.5 V$, and $I_v = 10 mA$. The frequency of oscillation is $f = 50 Hz$ and the width of the triggering pulse is $t_g = 50 \mu s$. Assume $V_D = 0.5 V$. (5 marks)

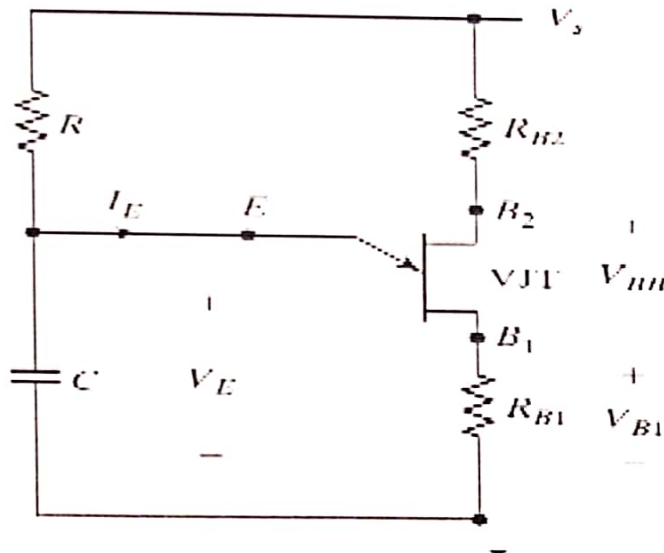


Fig. Q6a

- b) Use appropriate well-labelled diagram, highlighting the essential components, to explain the operation of
- Uninterruptible power supply (UPS) (3 marks)
 - High voltage direct current (HVDC) transmission system (4 marks)
- c) An HVDC transmission system is rated as $500 MW, \pm 250 kV$, determine the RMS current and peak reverse voltage of each thyristor. (3 marks)